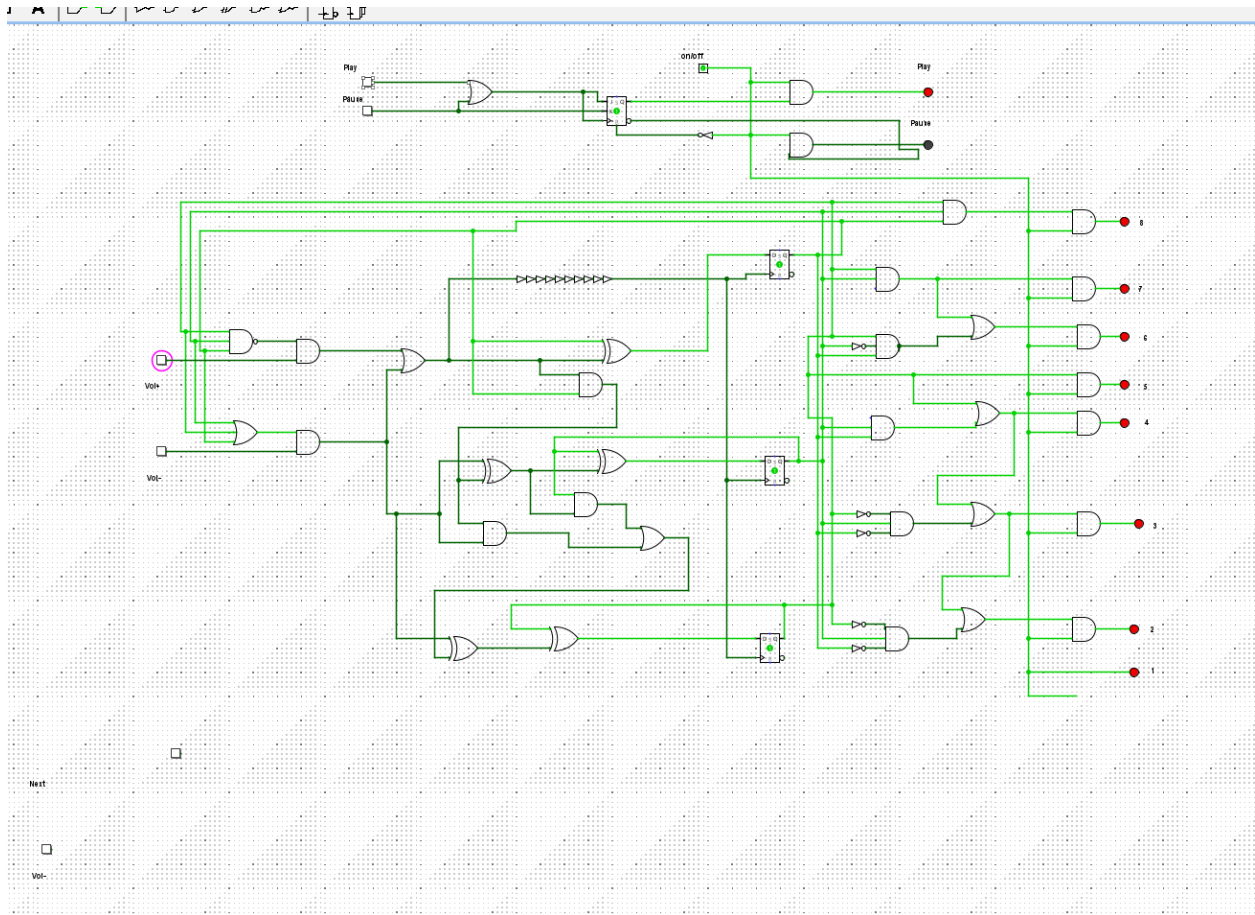


# Nguyen Manh Duc

## Lab06

### 1, My working so far



2, I think most challenging work is the next and previous function because the heavy use with hex display and 7 bit function so I don't have no idea what this may be like and the gates it include